

Circuit, State Diagram, State Table

Circuits with Flip-Flop = Sequential Circuit

Circuit = State Diagram = State Table


State Minimization

Sequential Circuit Design

Example: Sequence Detector

Example: Binary Counter


Circuit, State Diagram, State Table

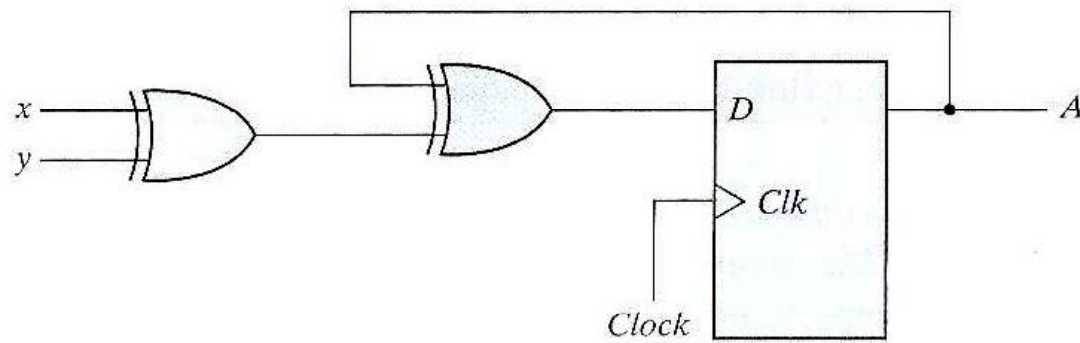

(a) Circuit diagram

FIGURE 5.17
Sequential circuit with D flip-flop

Circuit, State Diagram, State Table

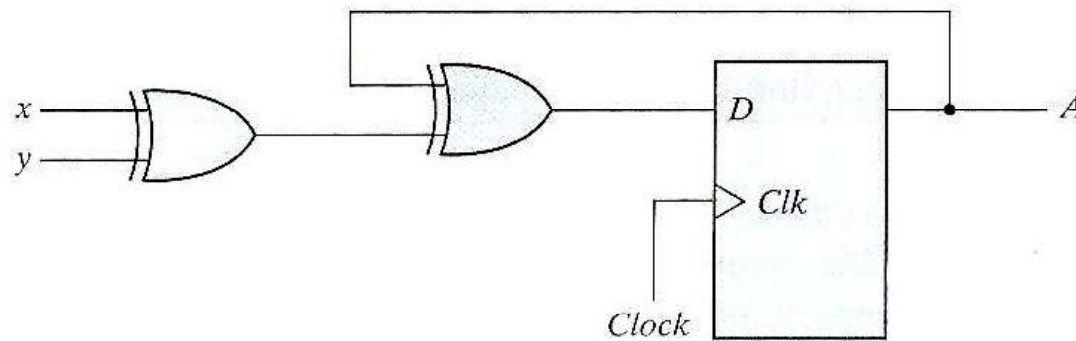


(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

FIGURE 5.17
Sequential circuit with D flip-flop


Circuit, State Diagram, State Table

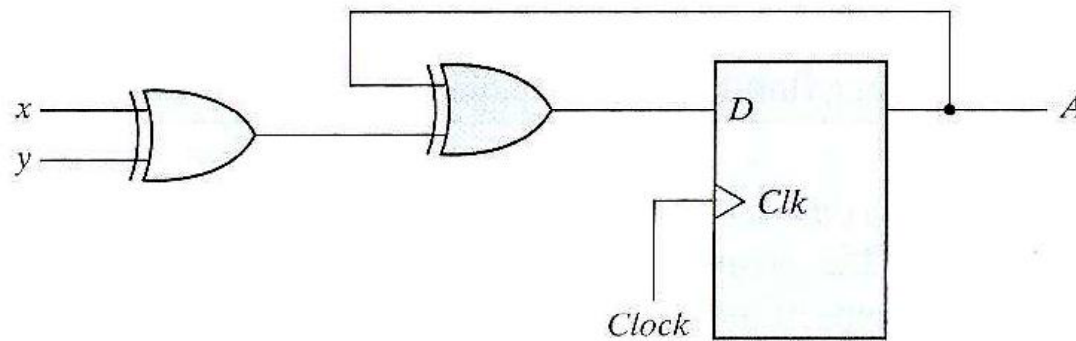

(a) Circuit diagram

Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(b) State table

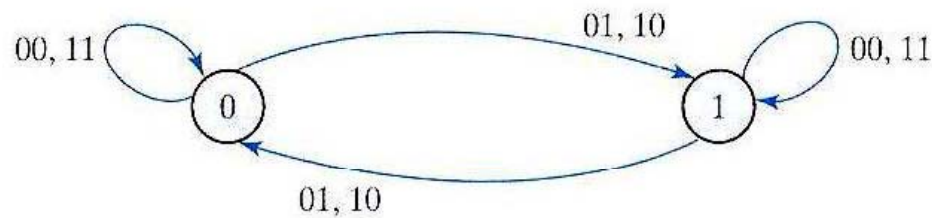

(c) State diagram

FIGURE 5.17
Sequential circuit with D flip-flop

Circuit, State Diagram, State Table

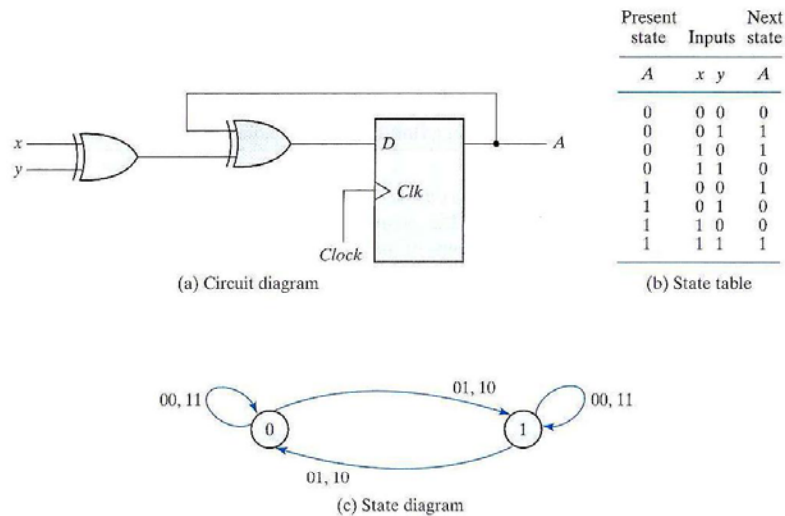


FIGURE 5.17
Sequential circuit with D flip-flop

Terms:

State: flip-flop output combination

Present state: before clock

Next state: after clock

State transition \leq clock

1 flip-flop \Rightarrow 2 states

2 flip-flops \Rightarrow 4 states

3 flip-flops \Rightarrow 8 states

4 flip-flops \Rightarrow 16 states

Circuit, State Diagram, State Table

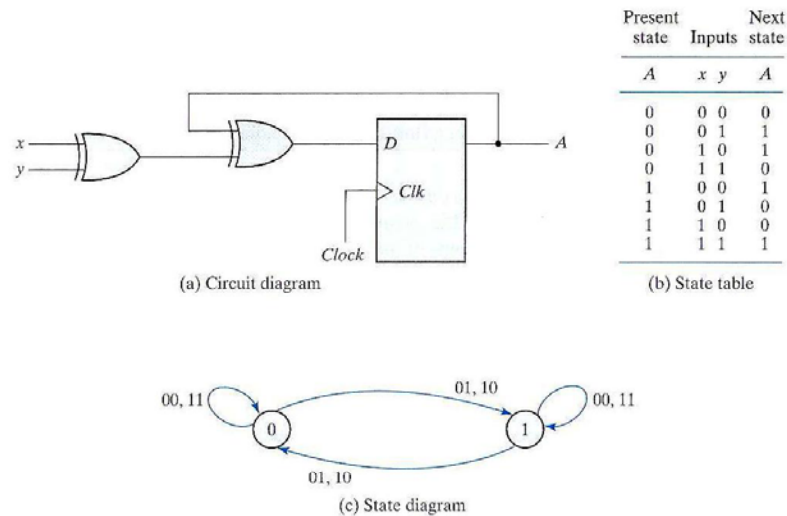


FIGURE 5.17
Sequential circuit with D flip-flop

Sequential circuit components:

Flip-flop(s)

Clock

Logic gates

Input

Output

Circuit, State Diagram, State Table

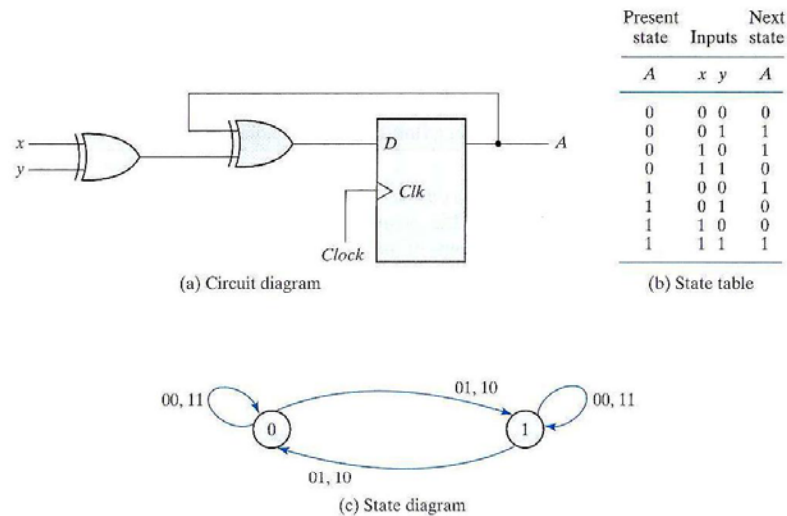


FIGURE 5.17
Sequential circuit with *D* flip-flop

State diagram:

Circle => state

Arrow => transition
input/output

Circuit, State Diagram, State Table

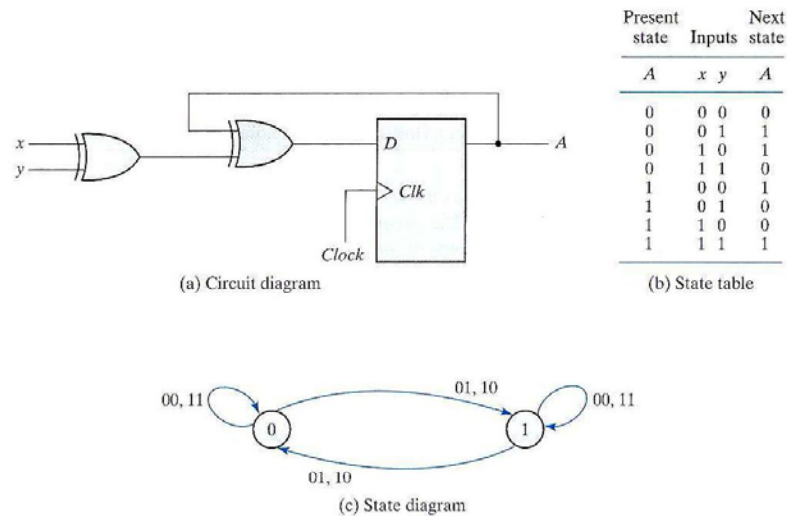


FIGURE 5.17
Sequential circuit with D flip-flop

State table:

Left column => current state

Top row => input combination

Table entry => next state, output

Circuit, State Table, State Diagram

Example:

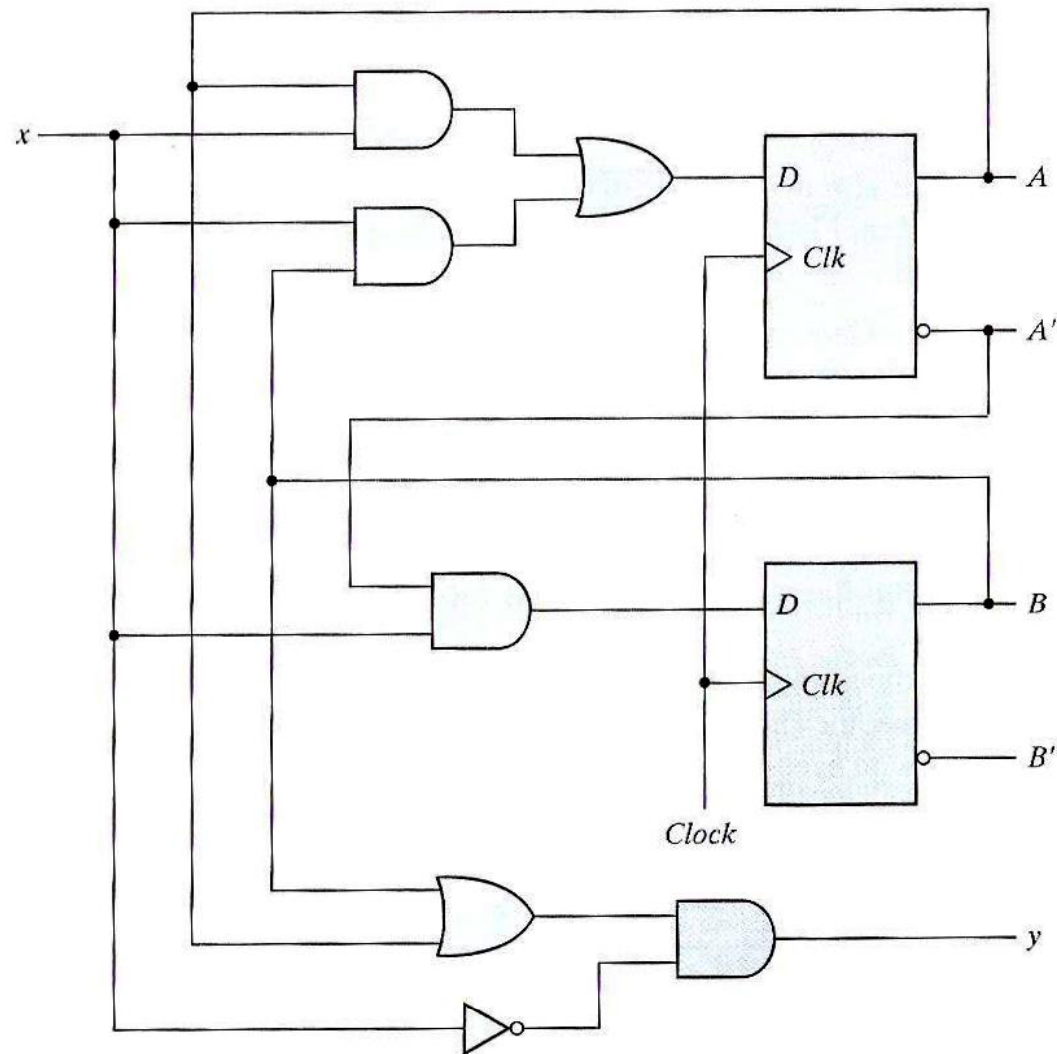


FIGURE 5.15
Example of sequential circuit

Circuit, State Table, State Diagram

Example: **Table 5.3**
Second Form of the State Table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

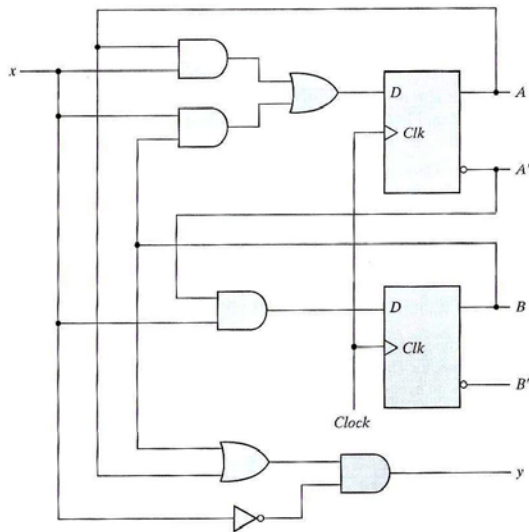


FIGURE 5.15
Example of sequential circuit

Circuit, State Table, State Diagram

Example:

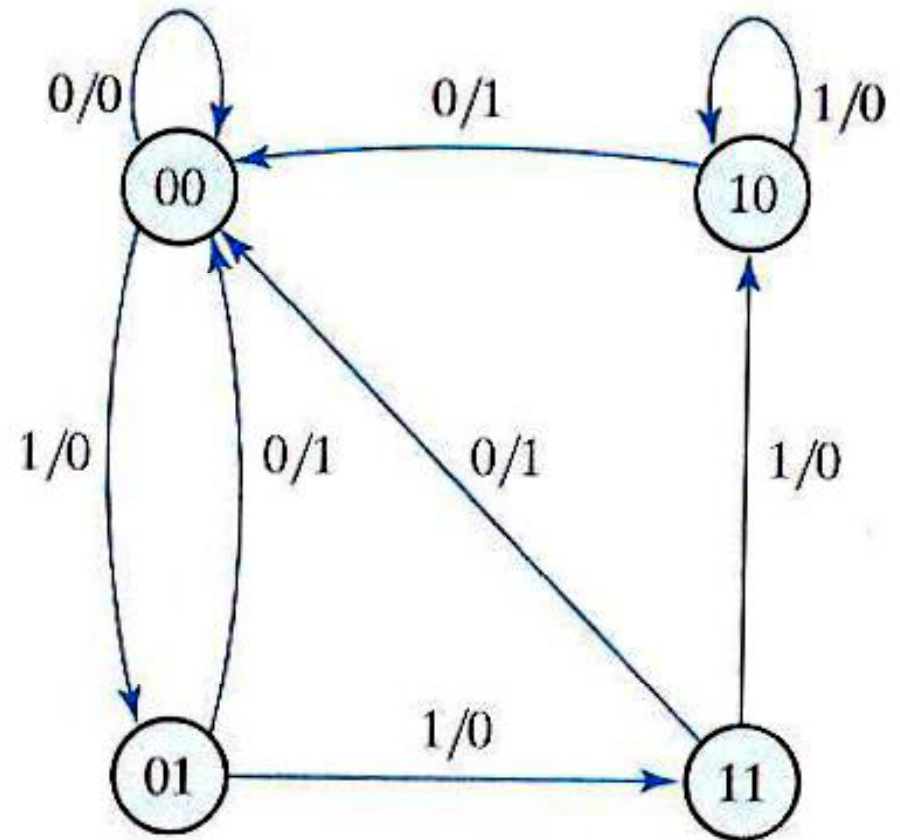


FIGURE 5.16

State diagram of the circuit of Fig. 5.15

Circuit, State Table, State Diagram

Example: **Table 5.3**
Second Form of the State Table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

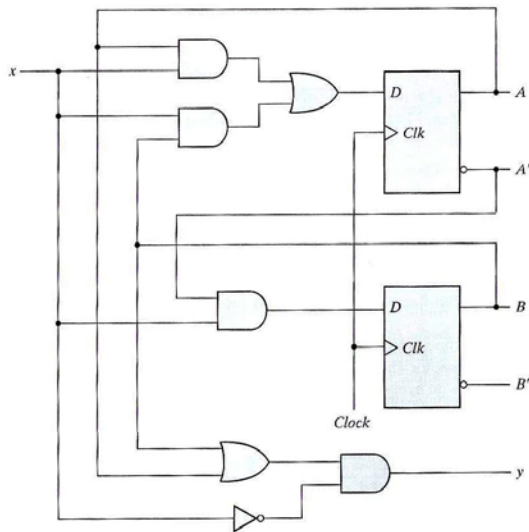


FIGURE 5.15
Example of sequential circuit


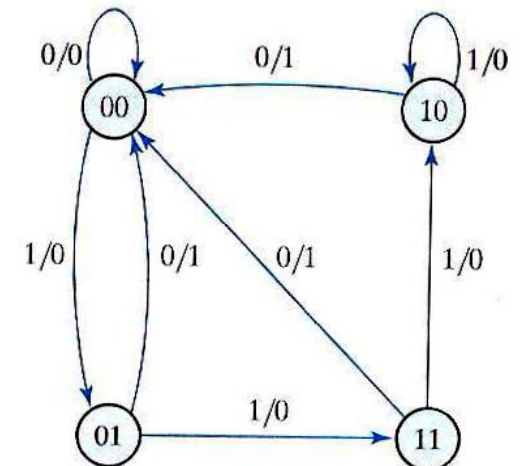


FIGURE 5.16
State diagram of the circuit of Fig. 5.15

Circuit, State Table, State Diagram


Example:

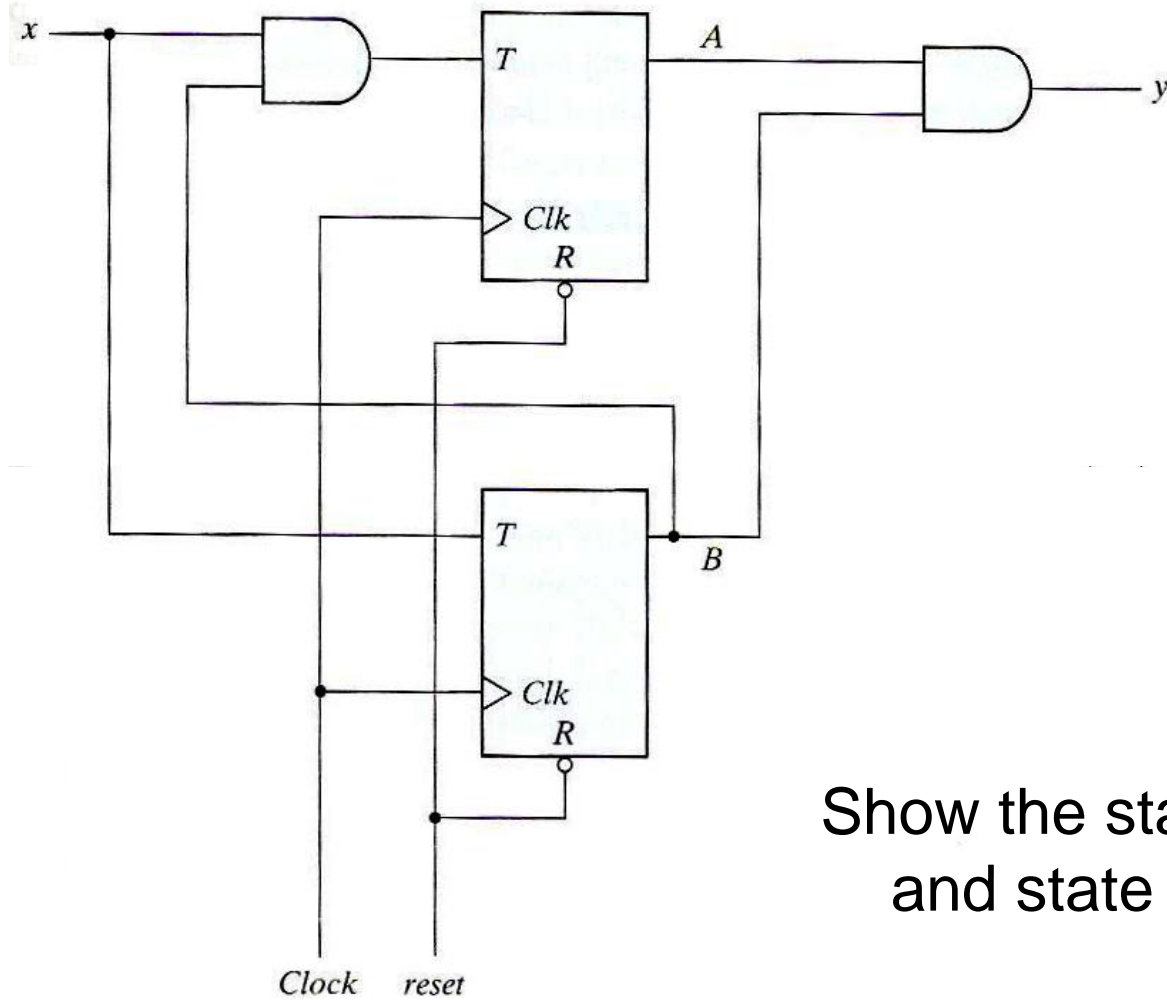

(a) Circuit diagram

Show the state table
and state diagram

FIGURE 5.20
Sequential circuit with T flip-flops


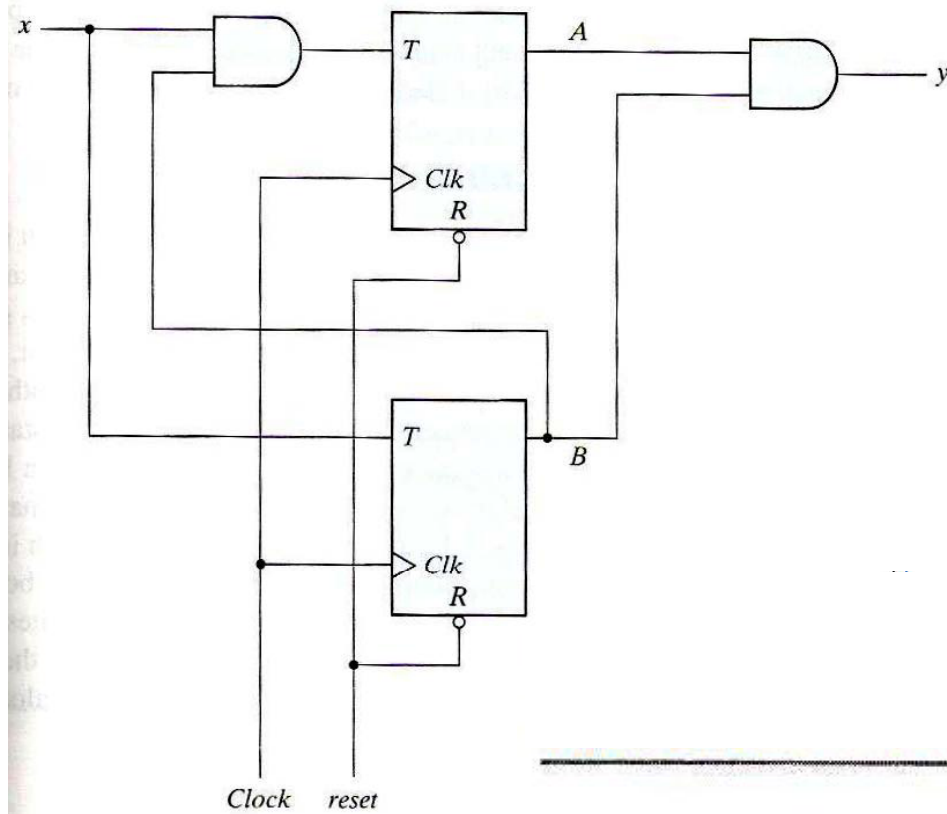


circuit

→ state table

→ state diagram

Present State		Next State				Output
		$x = 0$		$x = 1$		
A	B	A	B	A	B	y
0	0	0	0	0	1	0
0	1	0	1	1	0	0
1	0	1	0	1	1	0
1	1	1	1	0	0	1

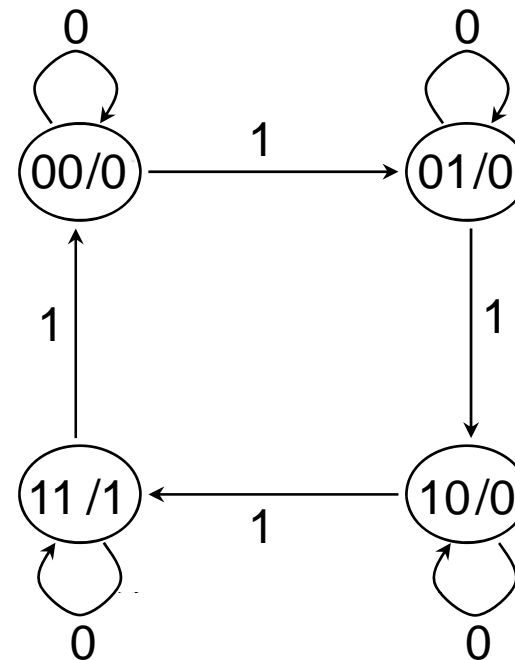
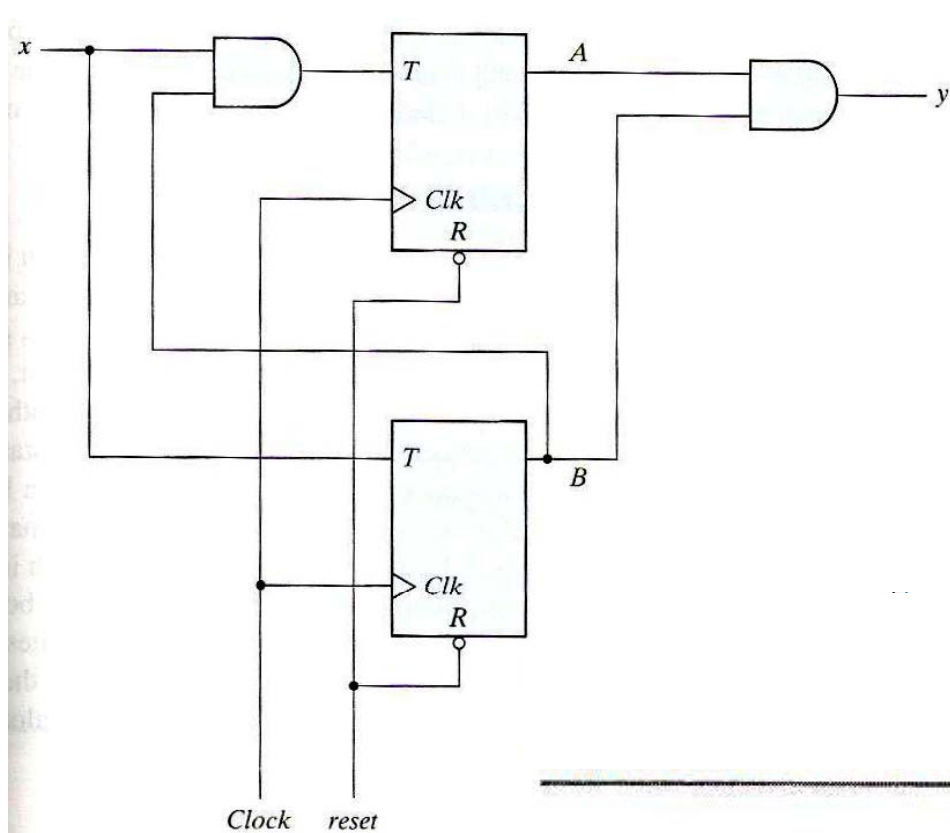


Present State		Next State				Output
		$x = 0$		$x = 1$		
A	B	A	B	A	B	y
0	0	0	0	0	1	0
0	1	0	1	1	0	0
1	0	1	0	1	1	0
1	1	1	1	0	0	1

circuit

→ state table

→ state diagram

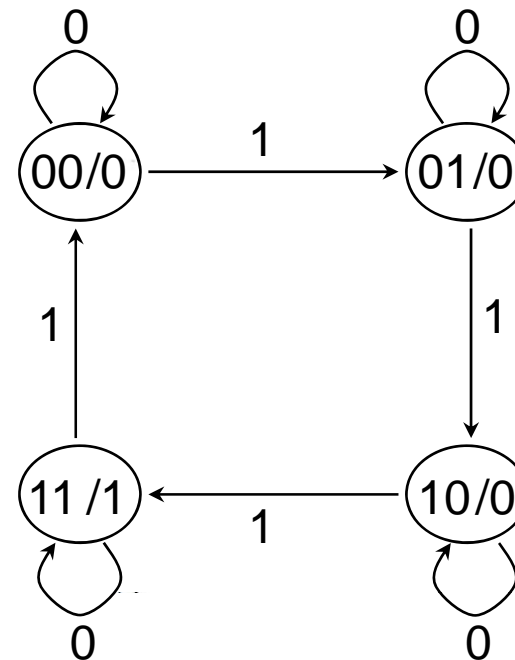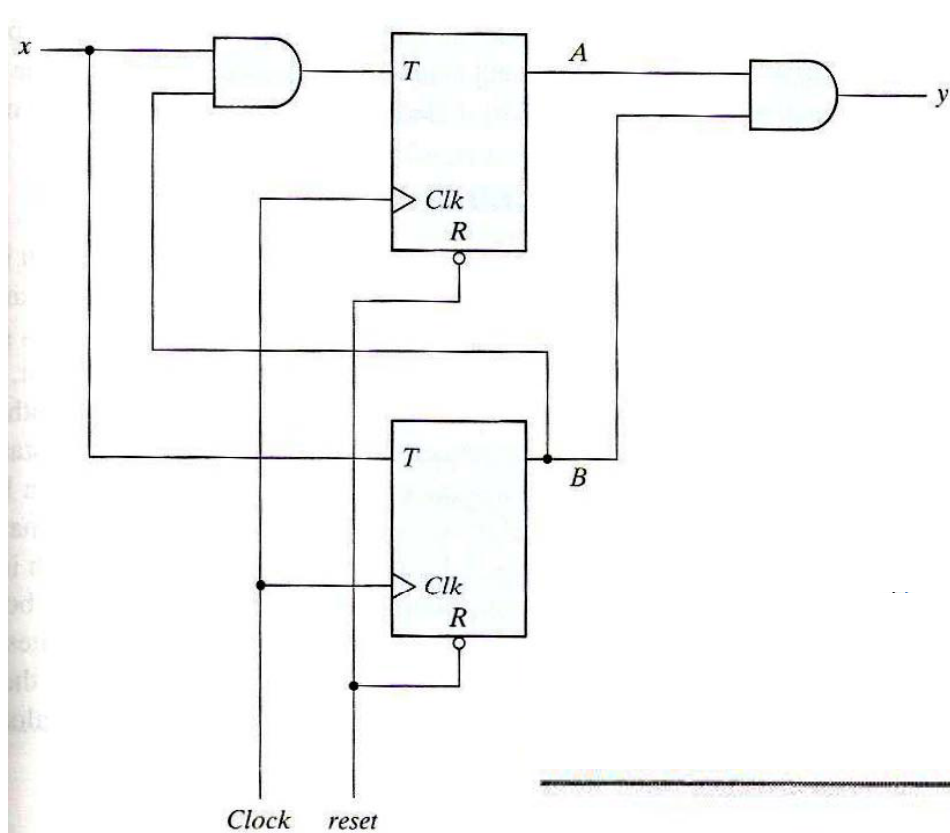

circuit


→ state table

→ state diagram


Present State		Next State				Output
		$x = 0$		$x = 1$		
A	B	A	B	A	B	y
		0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	0	0	1

Circuit, State Table, State Diagram

Example:

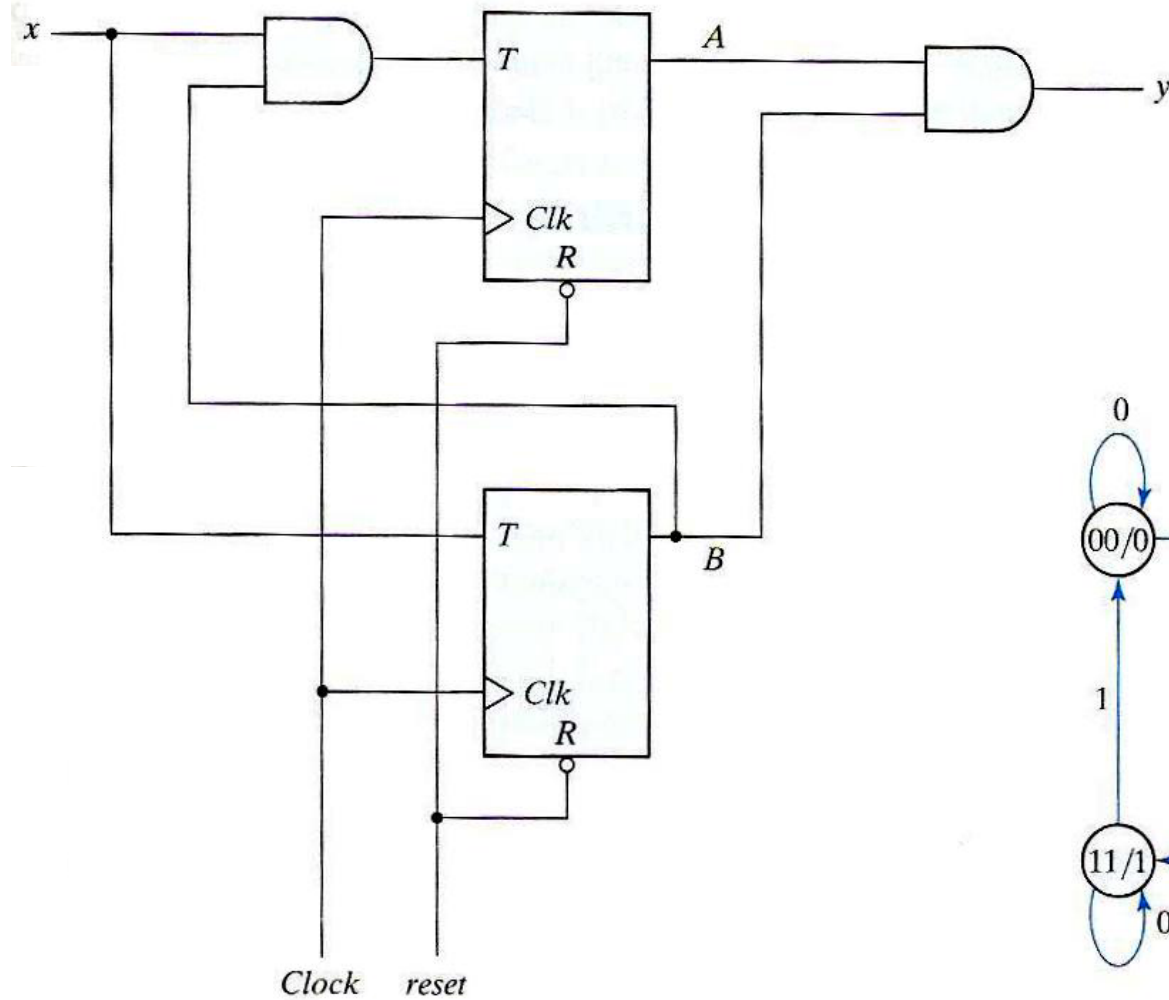

(a) Circuit diagram

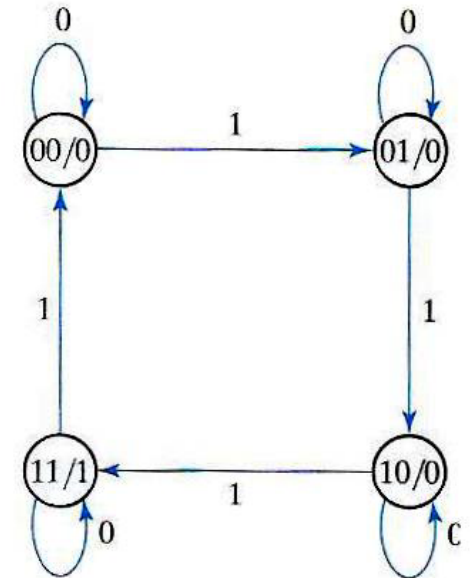


(b) State diagram

FIGURE 5.20
Sequential circuit with T flip-flops


Circuit, State Diagram, State Table

Example: state diagram = state table

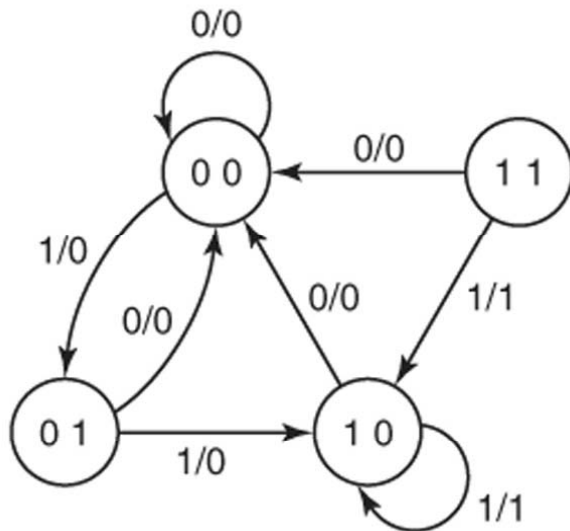

Circuit, State Diagram, State Table

Example: state diagram = state table

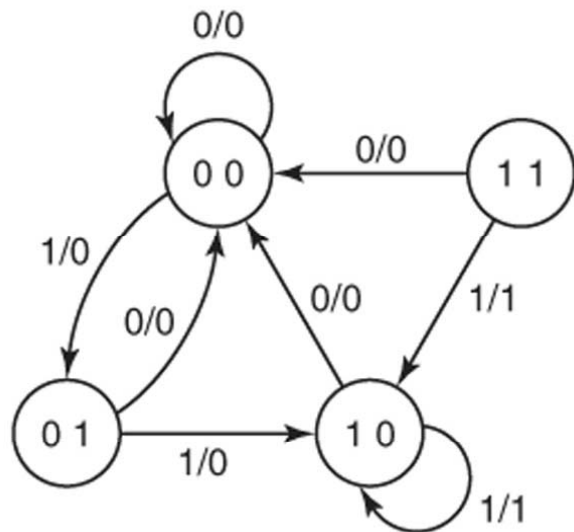

q	q^*		z	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	0	0
0 1	0 0	1 0	0	0
1 0	0 0	1 0	0	1
1 1	0 0	1 0	0	1

Circuit, State Diagram, State Table

Example: Show the state diagram of following circuit

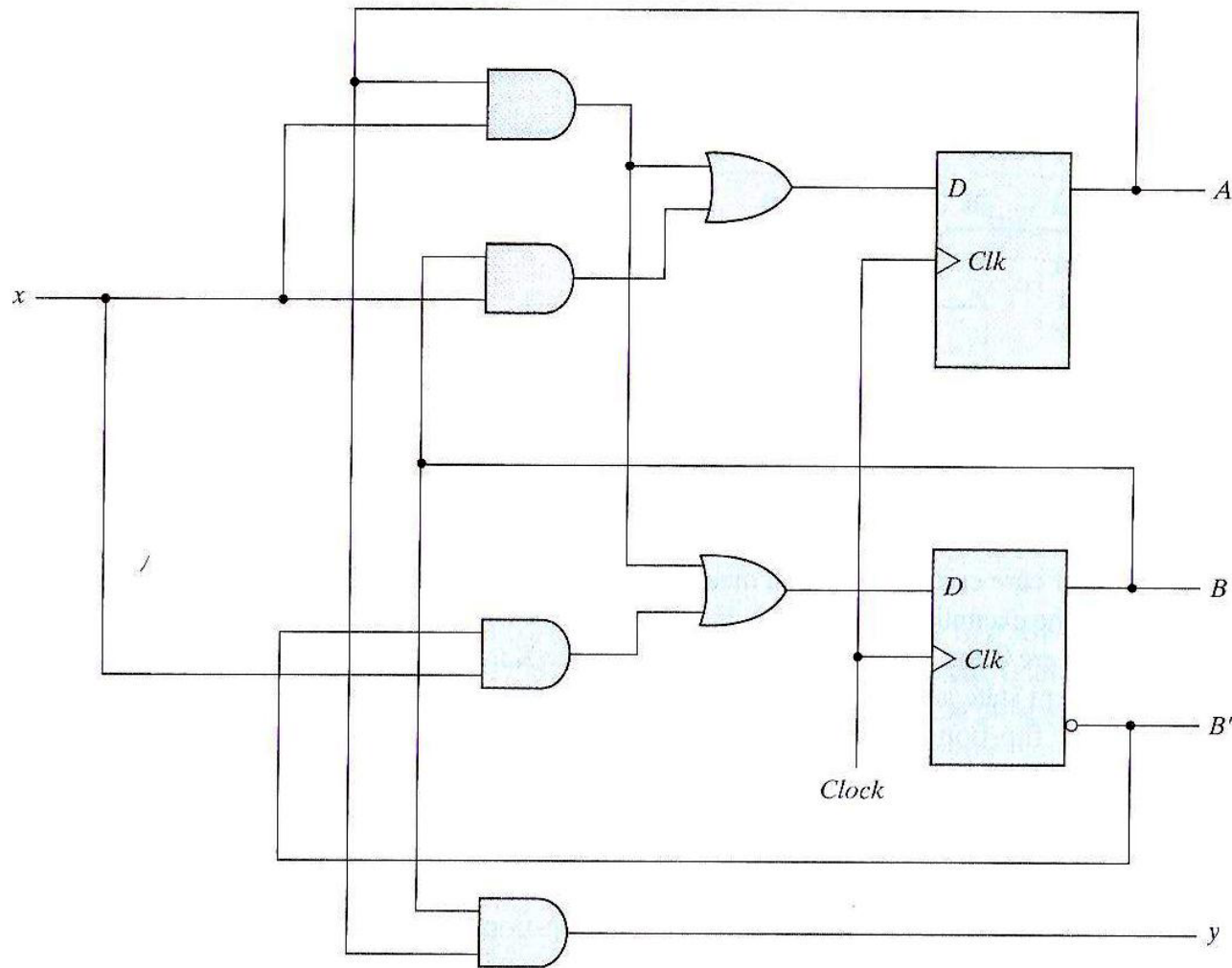


FIGURE 5.29
Logic diagram of sequence detector

Circuit, State Diagram, State Table

Example: Show the state diagram of following circuit

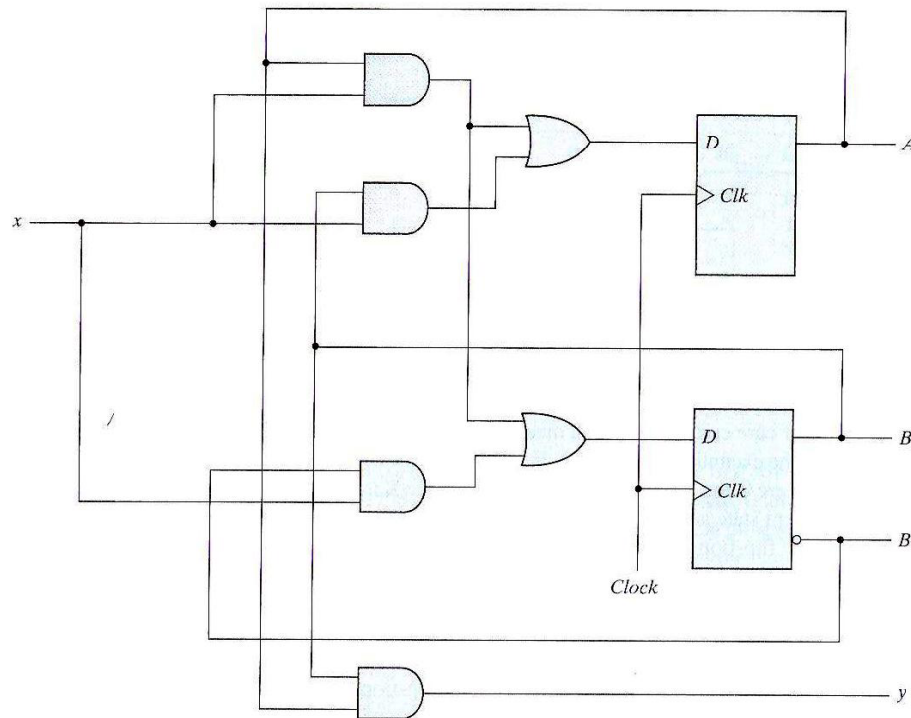


FIGURE 5.29
Logic diagram of sequence detector

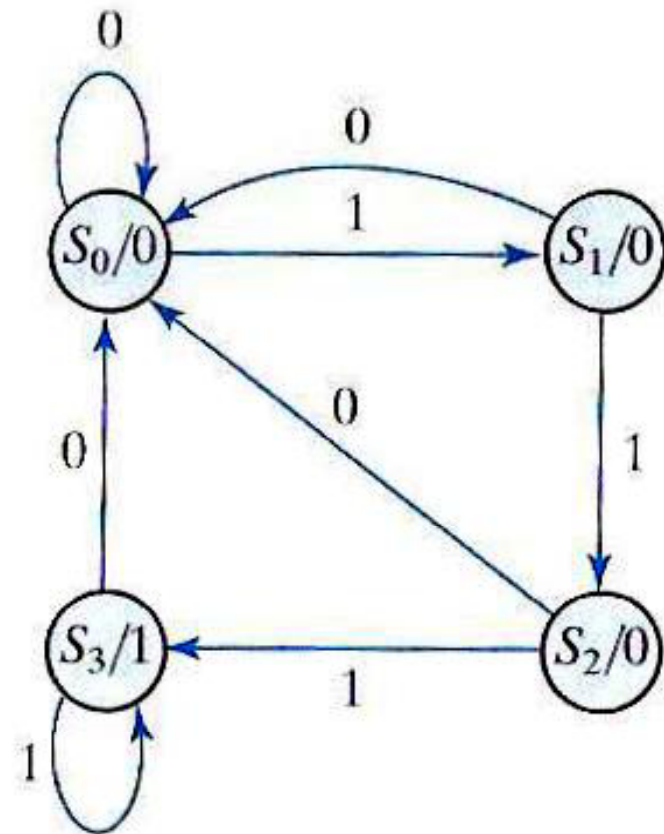


FIGURE 5.27
State diagram for sequence detector

Circuit, State Diagram, State Table

More Example: Binary Counter – show state diagram and table

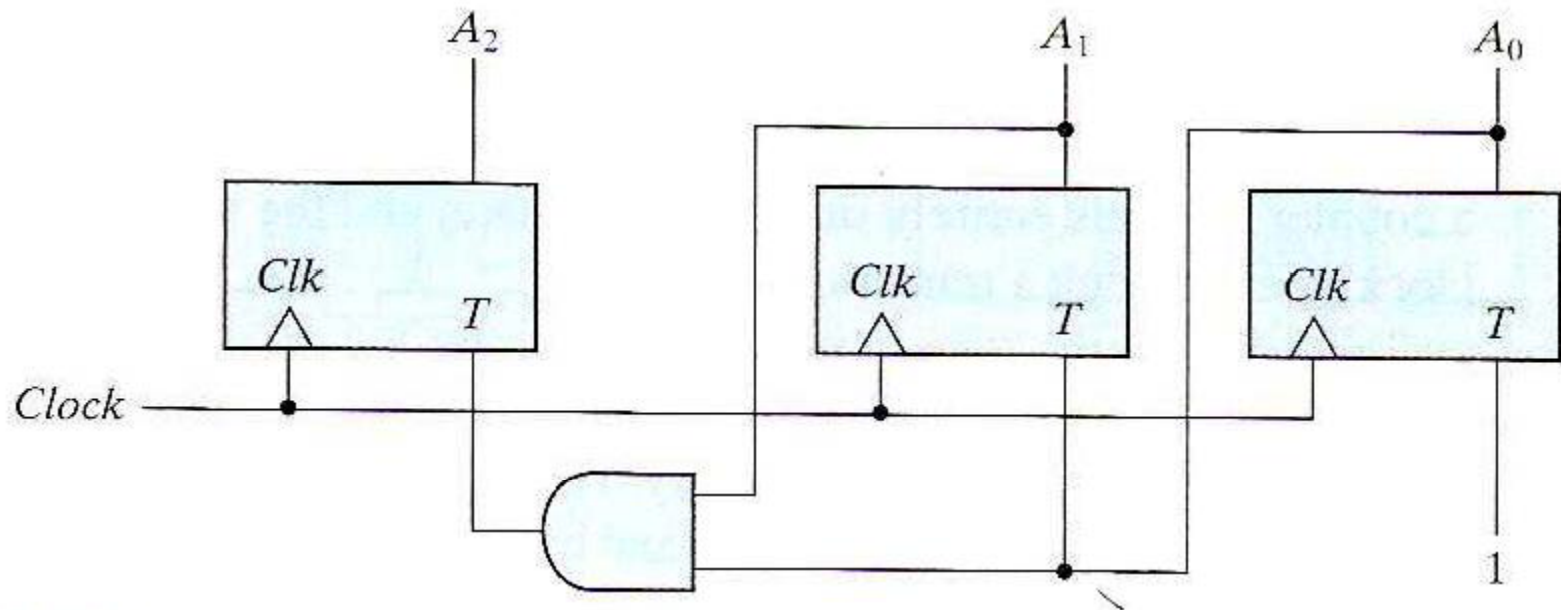


FIGURE 5.34

Logic diagram of three-bit binary counter

Circuit, State Diagram, State Table

More Example: Binary Counter – show state diagram and table

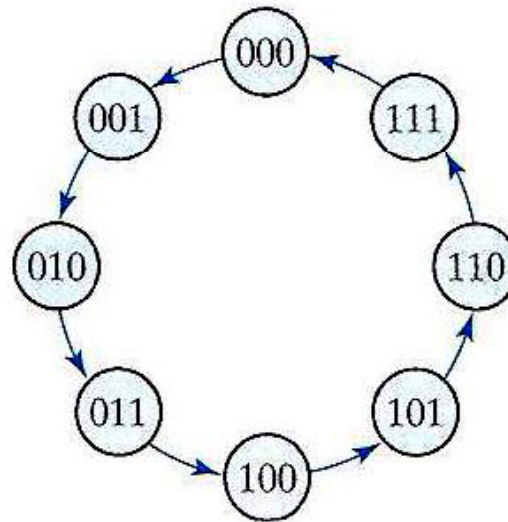


FIGURE 5.32
State diagram of three-bit binary counter

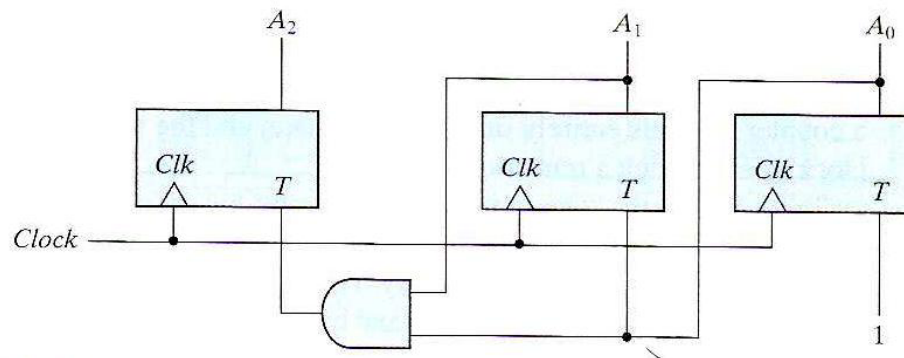


FIGURE 5.34
Logic diagram of three-bit binary counter

Circuit, State Diagram, State Table

Quiz:

http://www.eelab.usyd.edu.au/digital_tutorial/part3/t-diag.htm

Circuit, State Diagram, State Table

Quiz: solution

http://www.eelab.usyd.edu.au/digital_tutorial/part3/t-diag.htm

Circuit, State Diagram, State Table

More Example:

http://www.eelab.usyd.edu.au/digital_tutorial/part3/example1-1.htm

